



University College Dublin

An Coláiste Ollscoile, Baile Átha Cliath

PHYC20080 Fields, Waves and Light

Experiment No.3 Determination of the Resistivity of a Metal Alloy
Using a Wheatstone Bridge

4 March 2025

by Joana C.C. Adao (Student No. 23311051)

With Beau Etac

Tuesday 16.00-18.00 Slot
Nicki (Coordinator)

Contents

Abstract	2
1 Theory	2
1.1 Resistance	2
1.2 Wheatstone Bridge	4
1.2.1 Derivation of the Wheatstone Bridge Resistor Relation	4
2 Methodology	6
3 Results and Calculations	7
4 Conclusion	8
References	9
List of Figures	9
List of Tables	10
Appendix	10
Code	10

Abstract

The aim of this experiment was to determine the resistance of a metal alloy wire using a Wheatstone bridge setup. By balancing the current across this bridge and measuring the lengths associated with the resistors (at the point of balance), the resistance ratio formula was applied to find the unknown resistance of the metal alloy wire to be $1.99 \pm 0.14 \, \Omega$. With the found dimensions for the cross-sectional area, the resistivity of the metal alloy wire was then found to be $8.26 \times 10^{-7} \pm 1.24 \times 10^{-7} \, \Omega\text{m}$. While this result was determined to be closest to the resistivity expected from stainless steel, constantan was considered to be the more likely material of the wire due to its common use in electrical circuits. Errors in determining the resistivity likely arose from experimental errors when finding the unknown resistance of the wire. By ensuring the connections on the Wheatstone bridge were properly secured and by doing additional measurements of resistance accuracy on the values could be improved.

1 Theory

1.1 Resistance

Resistance (R) is a force that opposes the flow of current in a circuit [1, 2, 3]. It can be described as the difficulty the electric charge faces when travelling through a medium. [2] There are two types of materials that have opposing resistances [1]:

- **Conductors:** materials with little resistance where electrons travel through easily; for example copper and gold (as well as most metals).
- **Insulators:** materials where electrical charge finds difficulty passing through; for example wood and rubber.

These properties can be seen in electrical wires, with the current-carrying copper wire encased in an insulating rubber tube for safety.

Resistors are circuit components specifically made to counteract the flow of current in a circuit [4, 5, 2] (Figure 1). They can be used in an electrical circuit to control the amount of voltage and current flowing in it, which is used to ensure the circuit doesn't blow and to also correctly distribute the current/voltage flowing through the circuit [4, 2] The surplus of electrical energy flowing through a resistor is converted into heat energy which then dissipates [2].

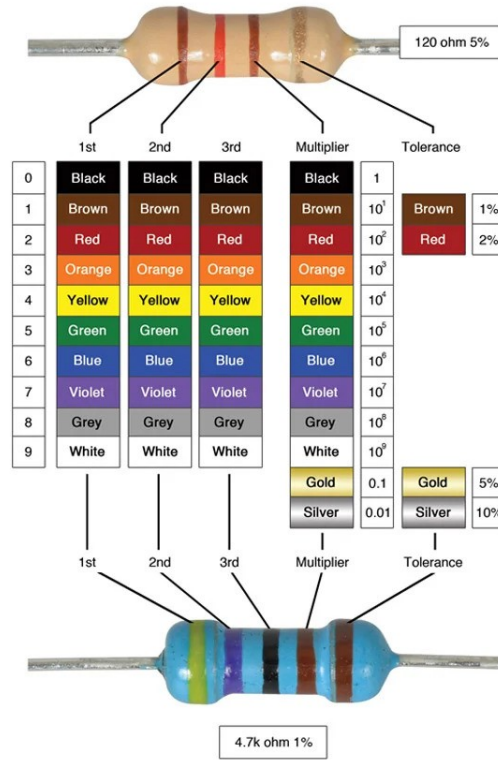


Figure 1: Image of resistor and guide on how to read it [6]

Resistors are used everywhere in day-to-day life as it is a basic circuit component. The most notable usages are for laptop (see figure 2) and phone chargers (see figure 3), which often have tens of resistors controlling the flow of the current to each different component of the laptop. Chargers often have the amount of current that specific charger allows the flow of, which is determined by the amount and type of resistor used [7].



Figure 2: Image of a laptop charger with resistor(s) highlighted [7].



Figure 3: Image of a phone charger with resistor(s) highlighted [7].

Resistivity (ρ) is a property of a material that describes how much that material opposes the flow of current through it. It is a property that is usually dependent on temperature or pressure rather than its physical factors (ie. shape, size, etc.).

The resistance depends on resistivity of a material, as well as length (L) and cross-sectional area (A). The equation for this relation is given below,

$$R = \frac{\rho L}{A} \quad (1)$$

As is seen, $R \propto L$, therefore if the length doubles the resistance will also double. In a similar but opposite fashion, $R \propto \frac{1}{A}$, therefore if the **radius** of the cross-sectional area doubles then the resistance will decrease proportionally by a factor of 4 as area is defined as $A = \pi r^2$.

1.2 Wheatstone Bridge

The Wheatstone bridge is a basic electrical circuit consisting of a power source, a **galvanometer** (G) (a highly sensitive ammeter), 3 resistors of known resistance and 1 resistor of unknown resistance (R_x) (see figure 4, 5). A Wheatstone bridge is just an instrument used to measure the resistance of the unknown resistor to high precision when it is compared to other resistors of known resistances [8, 9].

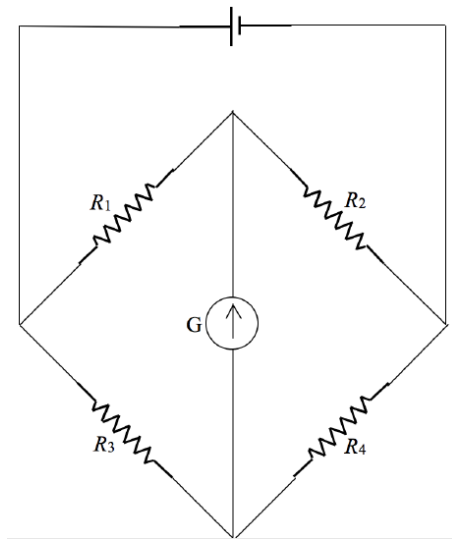


Figure 4: Diagram of a Wheatstone bridge setup [9].



Figure 5: Image of typical Wheatstone bridge instrument [8].

1.2.1 Derivation of the Wheatstone Bridge Resistor Relation

First, the wheastone bridge circuit is easier to understand when it is simplified and labelled (see figure 6):

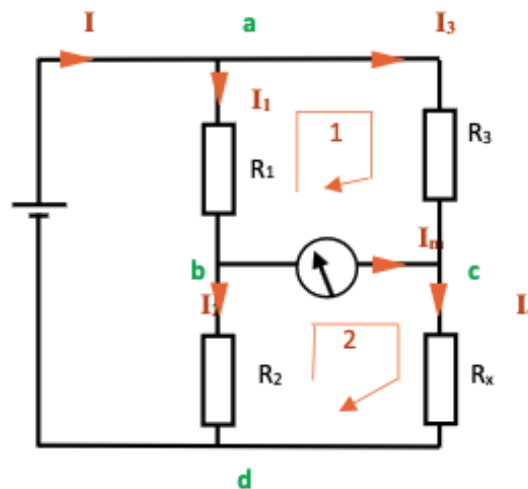


Figure 6: Simplified and labelled Wheatstone bridge diagram [10]

With the simplified circuit it is clear to see that the relation is consisted of series and parallel combinations. By application of Kirchoff's laws at each junction, the following is found (as junctions **a** and **d** consider just I):

$$\text{At junction } \mathbf{b}, \quad I_1 = I_2 + I_m \quad (2)$$

$$\text{At junction } \mathbf{c}, \quad I_4 = I_3 + I_m \quad (3)$$

With I_m as the current through the galvanometer and I_x ($x = 1, 2, 3, 4$) the current through each resistor. At loop 1 (involving resistors R_1 and R_3) and at loop 2 (involving resistors R_2 and R_x) the following can be understood:

$$\text{At loop 1,} \quad V_{R_1} - V_{R_3} + V_m = 0 \implies I_1 R_1 - I_3 R_3 + I_m R_m = 0 \quad (4)$$

$$\text{At loop 2,} \quad V_{R_2} - V_m - V_{R_x} = 0 \implies I_2 R_2 - I_m R_m - I_4 R_x = 0 \quad (5)$$

The positive/negative values taken for each component are dependent on whether the current flows in the same/opposite direction to the specified loop respectively. But the unknown resistance can only be found when the bridge is balanced, therefore $I_m = 0$,

$$(1) \implies I_1 = I_2$$

$$(2) \implies I_4 = I_3$$

As is expected with resistors in series. And the following can also then be said when $I_m = 0$,

$$(3) \implies I_1 R_1 = I_3 R_3$$

$$(4) \implies I_2 R_2 = I_4 R_x$$

But the new relationship for (2) and (3) can be used in (4) to find:

$$I_2 R_1 = I_4 R_3 \quad (6)$$

(6) can then be divided by (5) to get rid of the currents and thus the relationship between resistors in a *balanced* Wheatstone bridge is found:

$$\frac{R_1}{R_2} = \frac{R_3}{R_x} \quad (7)$$

(7) can be manipulated to solve for the unknown resistance, R_x :

$$R_x = R_3 \frac{R_2}{R_1} \quad (8)$$

2 Methodology

The apparatus was connected as shown in figure 7, with a metal alloy wire of unknown resistance connected to one of the bridges. For the simplicity of this experimental setup, the resistor relation in a wheatstone bridge can make use of the fact that $R \propto L$ to infer from (7),

$$\frac{R_1}{R_x} = \frac{L_1}{L_2} \quad (9)$$

The ratio difference between lengths associated with the respective resistors ($R_1 \propto L_1$, $R_x \propto L_2$) allows for the calculation of the unknown resistance.

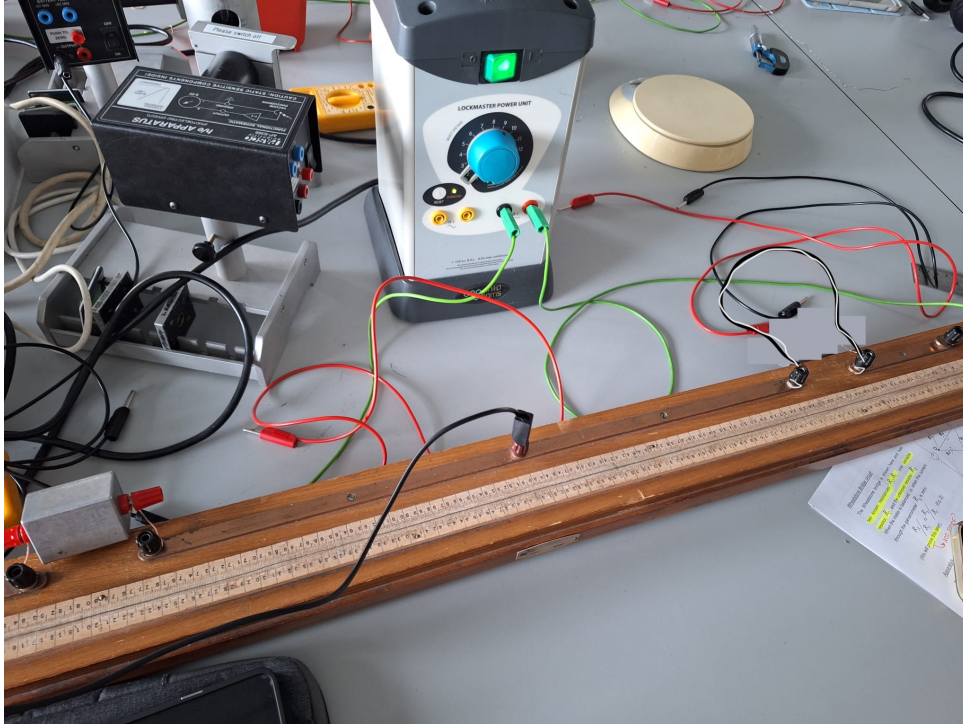


Figure 7: Image of the apparatus setup with wire alloy of unknown resistance drawn in.

The respective lengths of each resistor is measured from the point when the contact maker (manual galvanometer) is stable at 0 (no deflections, balanced). These measurements are recorded including the resistance of the known resistor.

The known resistance resistor and metal alloy wire of unknown resistance swap places in order to verify equipment is functioning. If results differ by more than 1 cm, it is likely that the meter bridge has poor contacts. This can be fixed by tightening the contacts at every point.

The average value for the unknown resistance is then found and the associated uncertainty by calculating the standard deviation.

The resistivity of the metal alloy wire can be found by using a micrometer to measure the average diameter of the wire (average of 6 measurements taken at different places) and using that value to find the average cross-sectional area. This calculated value can be plugged into equation 1 to then find the resistivity of the wire.

3 Results and Calculations

The known resistance resistor was chosen, at random, to be **0.97Ω**. After successfully connecting the metal alloy wire to the metre bridge, the system was found to be balanced at lengths 0.308 m (L_1) and 0.692 m (L_2). By equation (9) the unknown resistance R_x is found to be,

$$R_x = R_1 \frac{L_2}{L_1} = 0.97 \cdot \frac{0.692}{0.308} = \mathbf{2.18 \Omega}$$

So R_x is found to be **2.18Ω**. When the position of the metal alloy wire and resistor are switched, the lengths at which the bridge is balanced are found to be 0.322 m (L_1) and 0.678 m (L_2). Though these measurements differ by more than 1 cm the experiment was allowed to proceed with these values. By equation (9) again the unknown resistance R_x is now found to be,

$$R_x = R_1 \frac{L_2}{L_1} = 0.97 \cdot \frac{0.678}{0.322} = \mathbf{2.04 \Omega}$$

So R_x is found to be **2.04 Ω**. Taking the average between these two values, the unknown resistance R_x of the metal alloy wire is found to be **2.11 Ω**.

A similar process was done for the same metal alloy wire but with differing known resistance resistors. The follow table is then compiled with the results found and calculated:

Table 1: Table of the values gathered for length and the calculated respective R_x values.

R_1 (Ω)	L_1 (m)	L_2 (m)	R_x (Ω)
0.97	0.308	0.692	2.18
0.97	0.322	0.678	2.04
0.94	0.302	0.698	2.17
2.71	0.619	0.381	1.67
4.74	0.659	0.341	2.45
1.87	0.571	0.429	1.40

The average value of the above unknown resistances R_x is found to then be **1.99 Ω**. With a standard deviation value of 0.350, the standard error (SE, R_x) is found to be:

$$SE, R_x = \frac{\sigma}{\sqrt{N}} = \frac{0.350}{\sqrt{6}} = \mathbf{0.14 \Omega}$$

Therefore, the average resistance for the metal alloy wire R_x is found to be **1.99 ± 0.14 Ω**.

The resistivity of the metal alloy wire can then be found using this value. The average diameter of the wire is found to be 0.49 mm (from 0.45 mm, 0.50 mm, 0.55 mm, 0.45 mm, 0.45 mm, 0.55 mm) and the length of the wire is found to be 0.455 m. The average cross-sectional area of the wire is then calculated to be:

$$A = \pi r^2 = \pi \left(\frac{0.49 \times 10^{-3}}{2} \right)^2 = 1.90 \times 10^{-7} \text{ m}$$

So the average resistivity of the wire (at room temperature) can then be calculated by equation (1),

$$\rho = \frac{RA}{L} = \frac{(1.99)(1.90 \times 10^{-7})}{0.455} = \mathbf{8.26 \times 10^{-7} \Omega m}$$

The error on the resistivity can be found using error propagation:

$$\Delta\rho = \rho \left(\frac{\Delta R}{R} + \frac{\Delta A}{A} + \frac{\Delta L}{L} \right)$$

With this formula, the average resistivity of the metal alloy wire with the associated error is then found to be $\mathbf{8.26 \times 10^{-7} \pm 1.24 \times 10^{-7} \Omega m}$ (*refer to the Appendix for the calculations code*).

4 Conclusion

By carrying out this experiment the resistance of the metal alloy wire (unknown resistance) was found to be $\mathbf{1.99 \pm 0.14 \Omega}$ and the resistivity of the same wire was calculated to be $\mathbf{8.26 \times 10^{-7} \pm 1.24 \times 10^{-7} \Omega m}$. By comparing to a table of the found values of resistivities for different metals [11], the calculated value is closest to the resistivity of stainless steel ($\rho = 6.9 \times 10^{-7} \Omega m$), but the most probable material that the metal alloy wire was made of is constantan ($\rho = 4.9 \times 10^{-7} \Omega m$) (55% copper, 45% nickel) purely due to its common usage in electrical circuits. Neither of these values are within the calculated error of allowance for resistivity, so there were likely issues during the measurement of the resistances for the wire. Errors for those measurements of the unknown resistances were likely from poor or unstable connections of the Wheatstone bridge. This could be fixed by ensuring all of the connections are firmly secured and tightened. More measurements for the unknown resistance using more known resistors could have also improved accuracy.

References

- [1] Anon. (n.d.) What is resistance? [Accessed 30 January 2025]. [Online]. Available: <https://www.fluke.com/en-ie/learn/blog/electrical/what-is-resistance>
- [2] ——. (n.d.) What is resistance? Learn about the fundamentals of resistance, calculation methods, and resistors. [Accessed 30 January 2025]. [Online]. Available: <https://www.hioki.com/euro-en/learning/electricity/resistance.html>
- [3] R. Curley. (2025, January) resistance. [Accessed 30 January 2025]. [Online]. Available: <https://www.britannica.com/technology/resistance-electronics>
- [4] A. Tikkanen. (2024, December) resistor. [Accessed 30 January 2025]. [Online]. Available: <https://www.britannica.com/technology/resistor>
- [5] Anon. (n.d.) Resistance. [Accessed 30 January 2025]. [Online]. Available: <https://www.bbc.co.uk/bitesize/articles/z6n27yc#z7hddp3>
- [6] ——. (n.d.) Resistor Picture Credit. [Online]. Available: <https://www.jameco.com/Jameco/workshop/CircuitNotes/circuit-notes-resistors.html>
- [7] ——. (n.d.) Top 5 Practical Applications of Resistors in Our Daily Life. [Accessed 8 March 2025]. [Online]. Available: <https://ohmlaw.com/practical-applications-of-resistors-in-daily-life/>
- [8] ——. (n.d.) Wheatstone Bridge. [Accessed 8 March 2025]. [Online]. Available: <https://allen.in/jee/physics/wheatstone-bridge>
- [9] J. Tatum. (n.d.) Wheatstone Bridge. [Accessed 8 March 2025]. [Online]. Available: [https://phys.libretexts.org/Bookshelves/Electricity_and_Magnetism/Electricity_and_Magnetism_\(Tatum\)/04%3A_Batteries_Resistors_and_Ohm%27s_Law/4.11%3A___Wheatstone_Bridge](https://phys.libretexts.org/Bookshelves/Electricity_and_Magnetism/Electricity_and_Magnetism_(Tatum)/04%3A_Batteries_Resistors_and_Ohm%27s_Law/4.11%3A___Wheatstone_Bridge)
- [10] P. Sooriyan. (2025) PHYC20090 Assignment 1 Solutions. [Accessed 8 March 2025]. [Online]. Available: <https://brightspace.ucd.ie/d2l/le/lessons/297044/topics/3579889>
- [11] A. M. Helmenstine. (2024, May) Table of Electrical Resistivity and Conductivity. [Accessed 8 March 2025]. [Online]. Available: <https://www.thoughtco.com/table-of-electrical-resistivity-conductivity-608499>

List of Figures

1	Image of resistor and guide on how to read it [6]	3
2	Image of a laptop charger with resistor(s) highlighted [7].	3
3	Image of a phone charger with resistor(s) highlighted [7].	3
4	Diagram of a Wheatstone bridge setup [9].	4
5	Image of typical Wheatstone bridge instrument [8].	4
6	Simplified and labelled Wheatstone bridge diagram [10]	4
7	Image of the apparatus setup with wire alloy of unknown resistance drawn in. .	6
8	Code for calculations in §3.	10

List of Tables

- 1 Table of the values gathered for length and the calculated respective R_x values. . 7

Appendix

Code

```
import numpy as np

L = np.array([0.455, 0.455, 0.455, 0.455, 0.455, 0.455])
dL = np.array([0.0005, 0.0005, 0.0005, 0.0005, 0.0005, 0.0005])

R = np.array([2.18, 2.17, 1.67, 2.45, 1.40, 2.04])
aR = np.average(R)
dR = np.std(R)/np.sqrt(np.size(R))

print(aR, r"$\pm$", dR) # avg R and SE on R

r = (np.array([0.45, 0.45, 0.45, 0.50, 0.55, 0.55]) * 1e-3) /2
ar = np.average(r)

A = np.pi * (r)**2
aA = np.pi * (ar)**2

dA = np.std(A)/np.sqrt(np.size(A))

print(aA, r"$\pm$", dA) # avg A and SE on A

rho = (R*A)/L # for this to work on python had to add the resistance from
↳ switched wire position so the arrays were the same size
arho = np.average(rho)
drho = rho * ( (dR/R) + (dA/A) + (dL/L))
adrho = np.average(drho)

print(arho, r"$\pm$", adrho)
```

Figure 8: Code for calculations in §3.